

# Computer Architecture

---

## Lab 5: Verilog Basics 2




# Getting Started

- Open a web browser and go to <https://www.edaplayground.com/>
- Create an account with your university email
 
# Resettable D Flip-Flop

```
module flopr(input  logic      clk,  
             input  logic      reset,  
             input  logic [3:0] d,  
             output logic [3:0] q);  
  
    // synchronous reset  
    always_ff @(posedge clk)  
        if (reset) q <= 4'b0;  
        else      q <= d;  
  
endmodule
```




# Blocking vs. Nonblocking Assignment

- `<=` is nonblocking assignment
  - Occurs simultaneously with others
- `=` is blocking assignment
  - Occurs in order it appears in file


```
// Good synchronizer using
// nonblocking assignments
module syncgood(input logic clk,
                input logic d,
                output logic q);

     logic n1;
    always_ff @(posedge clk)
    begin
        n1 <= d; // nonblocking
        q  <= n1; // nonblocking
    end
endmodule
```



```
// Bad synchronizer using
// blocking assignments
module syncbad(input logic clk,
               input logic d,
               output logic q);

     logic n1;
    always_ff @(posedge clk)
    begin
        n1 = d; // blocking
        q  = n1; // blocking
    end
endmodule
```




# Rules for Signal Assignment

- **Synchronous sequential logic:** use `always_ff @ (posedge clk)` and nonblocking assignments (`<=`)  

```
always_ff @ (posedge clk)  
    q <= d; // nonblocking
```
- **Simple combinational logic:** use continuous assignments (`assign...`)  

```
assign y = a & b;
```
- **More complicated combinational logic:** use `always_comb` and blocking assignments (`=`)
- Assign a signal in **only one** `always` statement or continuous assignment statement.

# Lab Assignment

- Write a SystemVerilog code to implement a register file
- It has 32 32-bit registers and the register 0 should be always 0
- It has two read ports and one write port
- It has the following inputs and outputs
  - iClk (1 bit): clock (rising edge)
  - iReset (1 bit): reset signal
  - iRaddr1 (5 bits): the register number of read port 1
  - oRdata1 (32 bits): the output of read port 1
  - iRaddr2 (5 bits): the register number of read port 2
  - oRdata2 (32 bits): the output of read port 2
  - iWaddr (5 bits): the register number of the write port
  - iWdata (32 bits): the input data for the write port
  - iWe (1 bit): the write enable signal
- Use the testbench in the following slide
- Save and submit the link of your design to the Blackboard.
  - Click  in the bottom window to copy the URL of your design.

# Testbench

```

module testbench_regfile();
  logic clk;
  logic reset;
  logic [4:0] raddr1, raddr2, waddr;
  logic we;
  logic [31:0] wdata;
  logic [31:0] rdata1, rdata2;
  logic result;
  logic [31:0] regs[31:0];
  integer i;

  regfile dut(
    .iClk          (clk),
    .iReset        (reset),
    .iRaddr1       (raddr1),
    .iRaddr2       (raddr2),
    .iWaddr        (waddr),
    .iWe           (we),
    .iWdata        (wdata),
    .oRdata1       (rdata1),
    .oRdata2       (rdata2)
  );

  always // no sensitivity list, so it always executes
  begin
    clk = 1; #5; clk = 0; #5;
  end

  initial begin
    result = 1;
    $dumpfile("dump.vcd"); $dumpvars;
    reset = 0; #21;
    raddr1 = 0; raddr2 = 0; waddr = 0; we = 0; wdata = 0;
    for(i=0; i<32; i=i+1) regs[i]=0;
    reset = 1; #10;
    reset = 0; #10;
    for(i=0; i<32; i=i+1) begin
      waddr = i; we = 1; wdata = $random; regs[i] = wdata; #10;
    end
    waddr = 0; we = 0; wdata = 0;
    for(i=0; i<32; i=i+1) begin
      raddr1 = i; raddr2 = i; #1
      if(i==0) begin
        if(rdata1 != 0 | rdata2 != 0) begin
          $display("Read data from r0 failed");
          result = 0;
        end
      end else begin
        if(rdata1 != regs[i]) begin
          $display("Read data from port 1 at address %d failed %x %x", i, rdata1, regs[i]);
          result = 0;
        end
        if(rdata2 != regs[i]) begin
          $display("Read data from port 2 at address %d failed", i);
          result = 0;
        end
      end
    end
    #9;
  end
  if(result)      $display("SUCCESS!");
  else            $display("FAILURE!");
  #10; $stop;
end
endmodule

```