

Computer Architecture

Lab 6: Datapath



Getting Started

- Download alu.sv, regfile.sv, imem.sv and dmem.sv from Blackboard
- Open a web browser and go to <https://www.edaplayground.com/>

```
// instance of inverter
```


Structural Modeling – Better Way

```
module and3(input  logic a, b, c,  
            output logic y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input  logic a,  
            output logic y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input  logic a, b, c  
              output logic y);  
    logic n1;  
  
    and3 andgate(  
        .a      (a),  
        .b      (b),  
        .c      (c),  
        .y      (n1)  
    );  
    inv  inverter(  
        .a      (n1),  
        .y      (y)  
    );  
endmodule
```

Datapath for lw Instruction

 

Testbench

- Copy the following testbench code to “testbench.sv” on the left

```
module testbench_lw();
    logic clk;
    logic reset;
    logic regwrite;
    logic memwrite;
    logic [2:0] alucontrol;

    datapath dut(
        .iClk                (clk),
        .iReset              (reset),
        .iRegWrite            (regwrite),
        .iMemWrite            (memwrite),
        .iALUControl          (alucontrol)
    );

    always // no sensitivity list, so it always executes
    begin
        clk = 1; #5; clk = 0; #5;
    end

    initial begin
        $dumpfile("dump.vcd"); $dumpvars;
        reset = 0; #21;
        reset = 1; #10;
        regwrite = 1; memwrite = 0; alucontrol = 3'b010;
        reset = 0; #10;

        #10; $stop;
    end
endmodule
```

Datapath

- Copy the following code to "design.sv" on the right

```
`include "alu.sv"
`include "regfile.sv"
`include "imem.sv"
`include "dmem.sv"


module datapath(
    input logic iClk,
    input logic iReset,
    input logic iRegWrite,
    input logic iMemWrite,
    input logic [2:0] iALUControl
);

endmodule
```

Building Blocks

- Click "+" right after "design.sv"
- Upload "alu.sv"
- Upload regfile.sv, imem.sv, and dmem.sv in the same way

Lab Assignment

- Finish the implementation of the datapath module
 - Implement the program counter and sign extension
 - Connect modules
- Save and submit the link of your design to the Blackboard.
 - Click  in the bottom window to copy the URL of your design.

Expected Result

